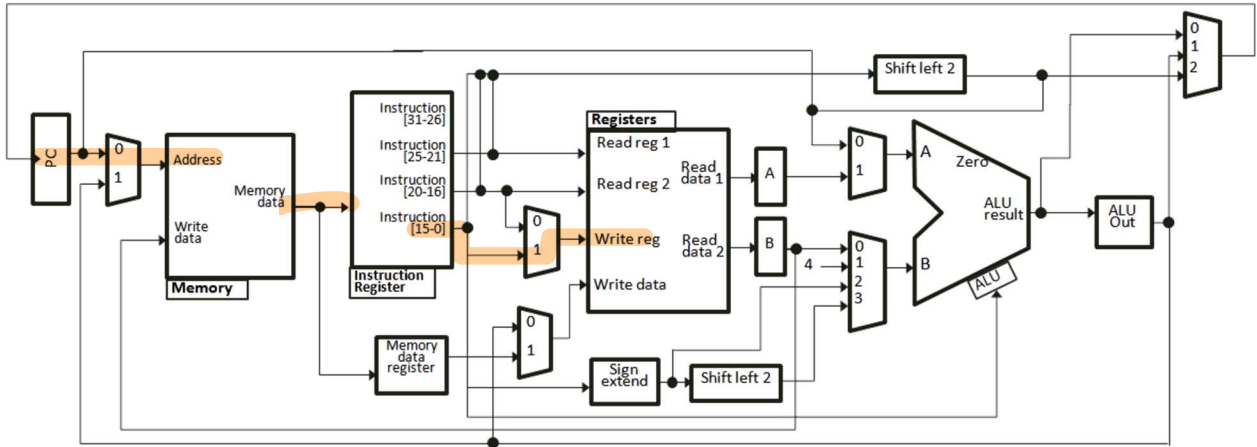


Part I: Processors, part 3 (12 marks)

Consider the datapath diagrams below. For each of the following operations, highlight the path(s) on the diagram that data will travel in implementing these operations. (4 marks each)


a) Store the program counter in the **return address register**.

sw \$ra, 0(\$sp)



b) Set \$t0 to zero.

add \$t0, \$zero

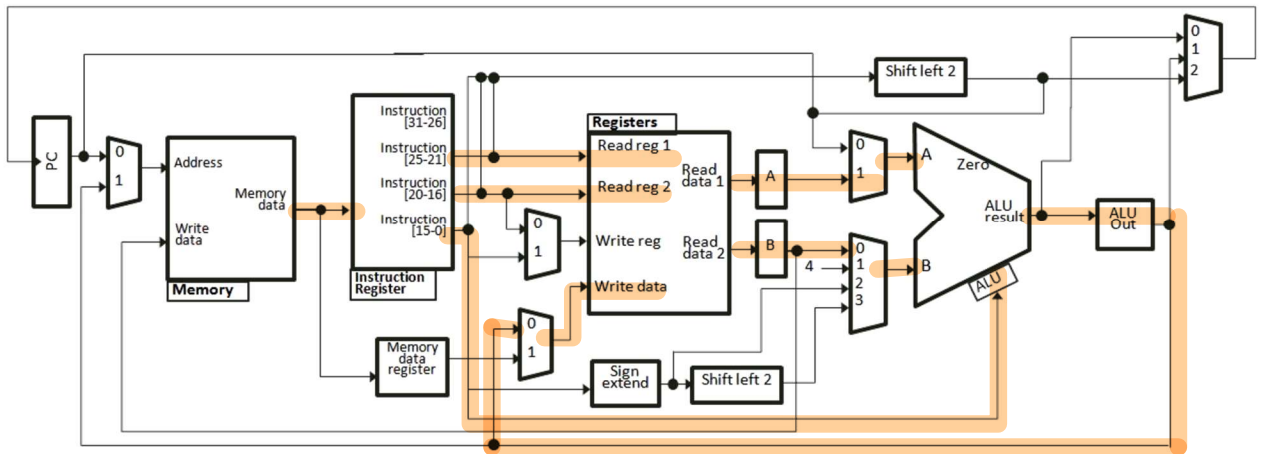

c) Fetch the top element from the stack and store it in \$t0.

lw \$t0, 0(\$sp)

